

# EE 316 Lab 6 Cover Sheet

**Name:** Vivian Tan

**EID:** vyt73

**Section:** 16050

**Design Problem:** 10.6 and 17.F

Part 1:

1. Block Diagram and VHDL code
2. Snapshot of output waveform with given inputs


Part 2:

3. VHDL code
4. Snapshot of output waveform with the same test inputs used in Lab 5

Signatures of the TA:

# 1. Block Diagram and VHDL code

## Block Diagram:

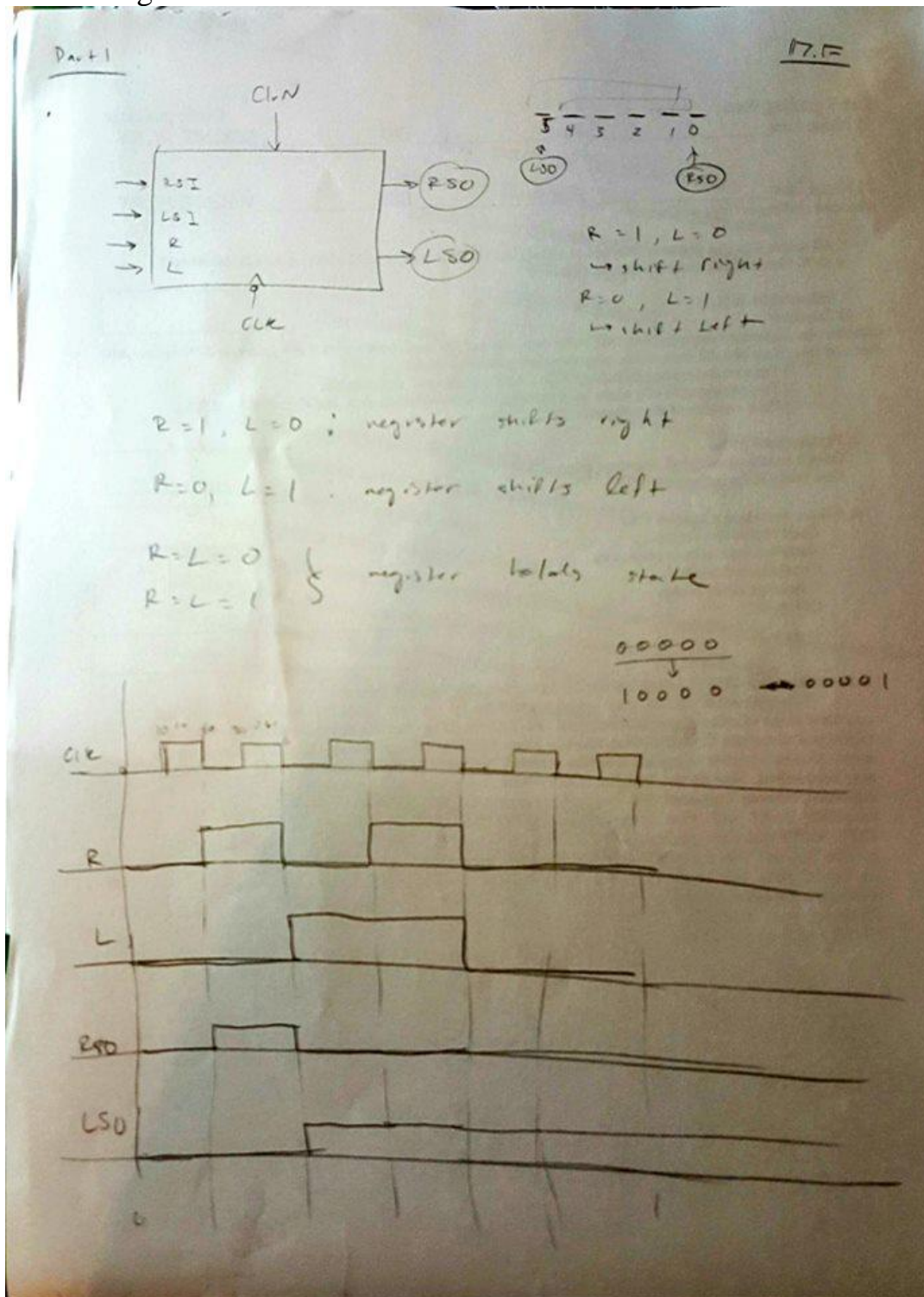


## VHDL:

```
library ieee;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

Entity shift is
    Port(CLK, LSI, RSI, R, L, ClrN: in std_logic;
          RSO, LSO: out std_logic);
End shift;

Architecture shiftarch of shift is
    signal temp: std_logic_vector(5 downto 0) := (Others => '0');
    --    if(ClrN = '0') then
    --        temp <= 0;
    --    end if;
    begin
        process(CLK, ClrN)
        begin
            if(ClrN = '0') then
                temp <= (others => '0');
            elsif(CLK'event and CLK = '1') then
                if(R = '1' and L = '0') then
                    temp <= RSI & temp(5 downto 1);
                elsif(R = '0' and L = '1') then
                    temp <= temp(4 downto 0) & LSI;
                end if;
            end if;
        end process;
        RSO <= temp(5);
        LSO <= temp(0);
    end shiftarch;
```

## 2. Snapshot:

 

### 3. VHDL Code:

```
library ieee;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity SM is
    Port(rst, clk, X: in std_logic;
          Q1, Q2, Q3, Z: out std_logic);
end SM;

architecture archsm of sm is
    signal state, nextstate: integer range 0 to 5 := 0;
    signal state_output: std_logic_vector(2 downto 0);

begin
    state_output <= conv_std_logic_vectOr(state, 3);
    Q3 <= state_output(2);
    Q2 <= state_output(1);
    Q1 <= state_output(0);

    process(state, X)
    begin
        case State is
            when 0 =>
                if X = '0' then Z<= '0'; nextstate <= 4;
                else Z <= '0'; nextstate <= 1; end if;
            when 1 =>
                if X = '0' then Z<= '0'; nextstate <= 2;
                else Z <= '0'; nextstate <= 1; end if;
            when 2 =>
                if X = '0' then Z<= '0'; nextstate <= 5;
                else Z <= '0'; nextstate <= 3; end if;
            when 3 =>
                if X = '0' then Z<= '1'; nextstate <= 2;
                else Z <= '0'; nextstate <= 1; end if;
            when 4 =>
                if X = '0' then Z<= '0'; nextstate <= 5;
                else Z <= '0'; nextstate <= 1; end if;
            when 5 =>
                if X = '0' then Z<= '0'; nextstate <= 5;
                else Z <= '0'; nextstate <= 5; end if;
        end case;
    end process;

    process(clk, rst)
    begin
        if (rst = '0') then
            state <= 0;
        elsif clk'event and clk = '1' then --rising edge
            state <= nextstate;
        end if;
    end process;
end archsm;
```

#### 4. Snapshots:

(1)  $X = 101011101001$   
 $Z = 000100000100$

(2)  $X = 010101001010$   
 $Z = 000010100000$

(1)



(2)

